

Analysis of the effect of system parasitic parameters on the switching of SiC devices

Wu Qibin, Infineon

Table of contents

1

Switch on current overshoot

2

Switching current oscillation

3

Effect of parasitic capacitance

4

Effect of parasitic inductance

5

Summary

Table of contents

1

Switch on current overshoot

2

Switching current oscillation

3

Effect of parasitic capacitance

4

Effect of parasitic inductance


5

Summary

SIC-MOS turn-on process with different continuum diodes


- Even if a Schottky diode is used, there is a turn-on current overshoot like reverse recovery

SIC MOS + SI Diode

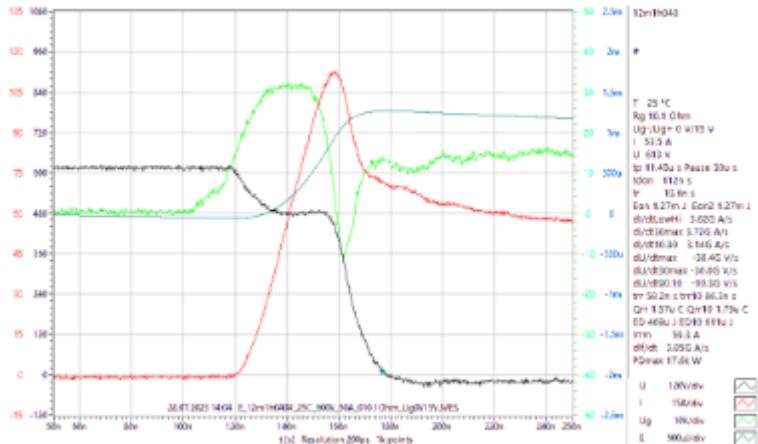


IMW120R040M1H+ 1200V 50A CH7 for reverse parallel Si Diode
RT, Rg on/off 10ohm/600VDC/ 50A /

SIC MOS + SIC Body Diode

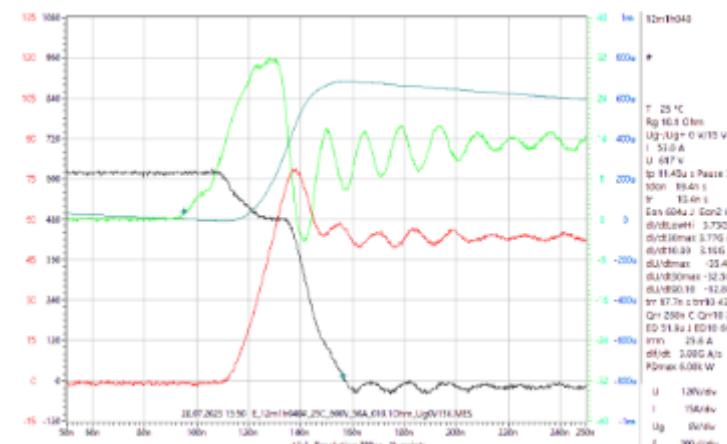

IMW120R040M1H+ IMW120R040M1H body SiC diode
RT, Rg on/off 10ohm/600VDC/ 50A /



SIC MOS + SIC Schottky Diode

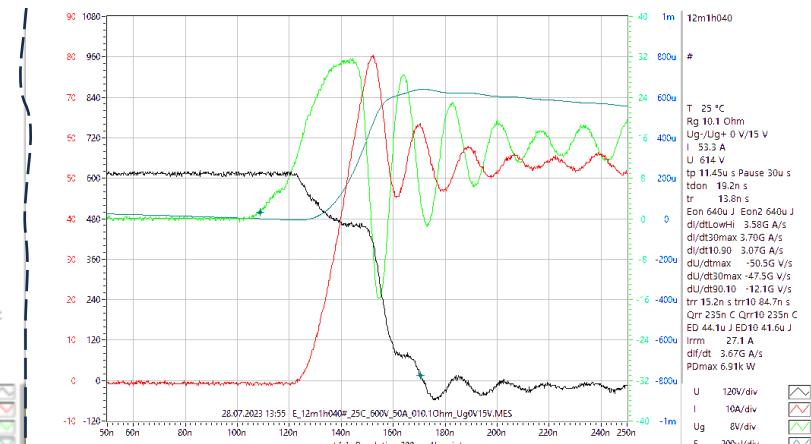

IMW120R040M1H+ 1200V 30A SiC Schottky diode
RT, Rg on/off 10ohm/600VDC/ 50A /

SPICE model-based simulation of SIC-MOS turn-on

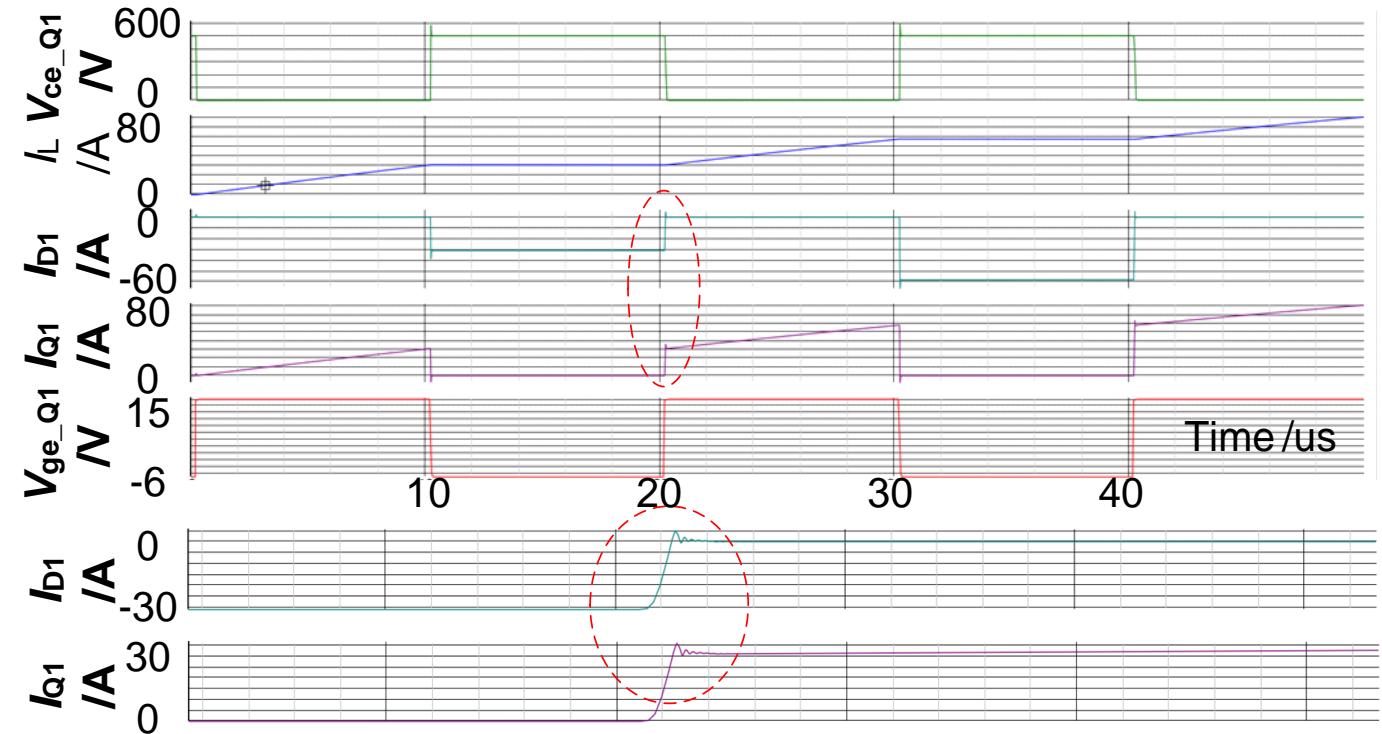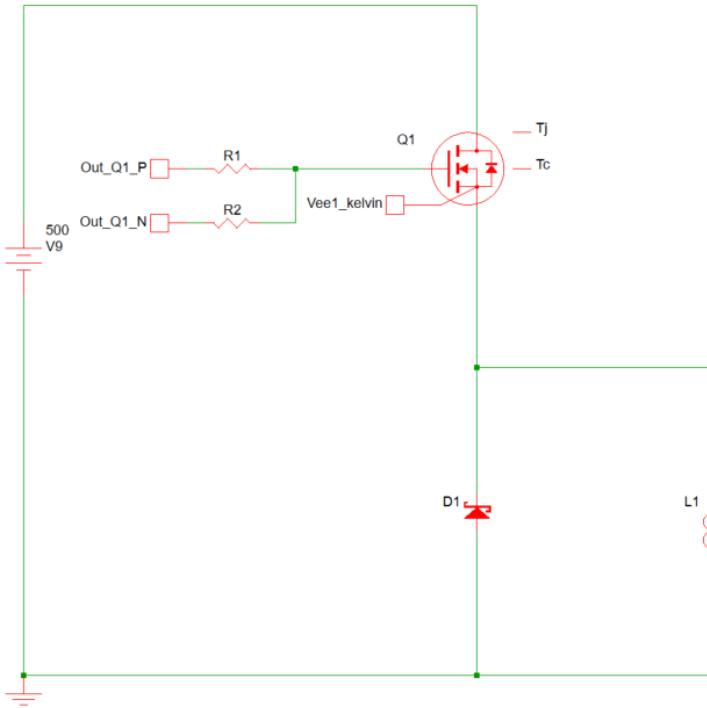- Simulations based on the Spice model also observe this current overshoot like reverse recovery





SPICE model-based simulation of SiC-MOS turn-on

- Effect of parasitic capacitance of the freewheeling diode


Parasitic capacitance parameters of IDW30G120C5B

Parameter	Symbol	Conditions	Value	Unit
Total Capacitance	C	$V_R=1V, f=1MHz$	990/1980	pF
		$V_R=400V, f=1MHz$	70/140	
		$V_R=800V, f=1MHz$	55/111	

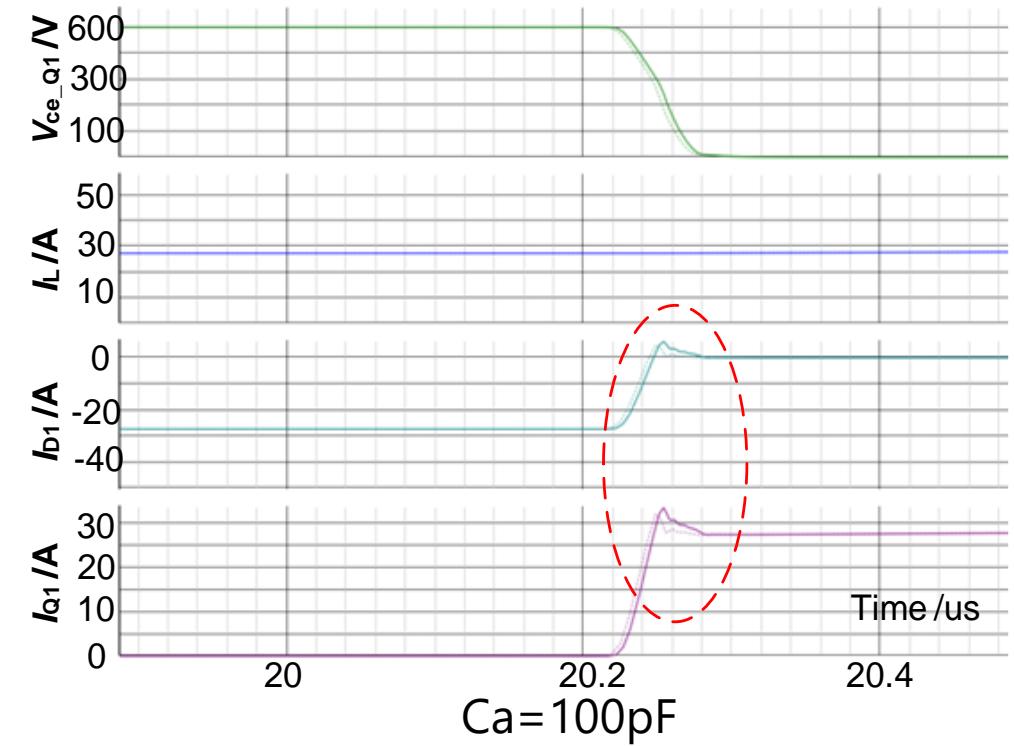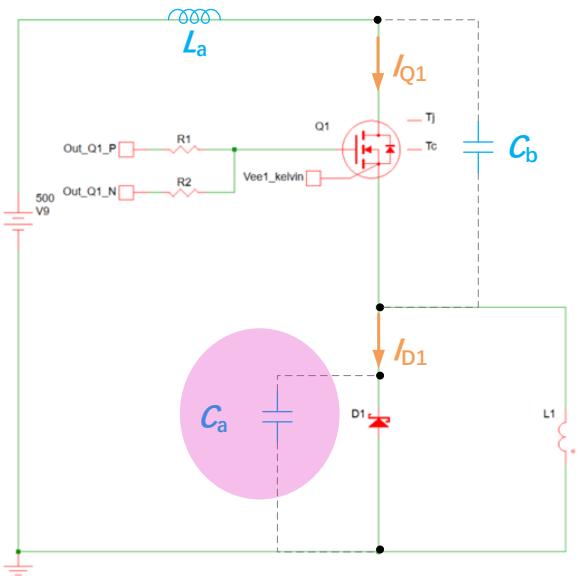

SPICE model-based simulation of SIC-MOS turn-on

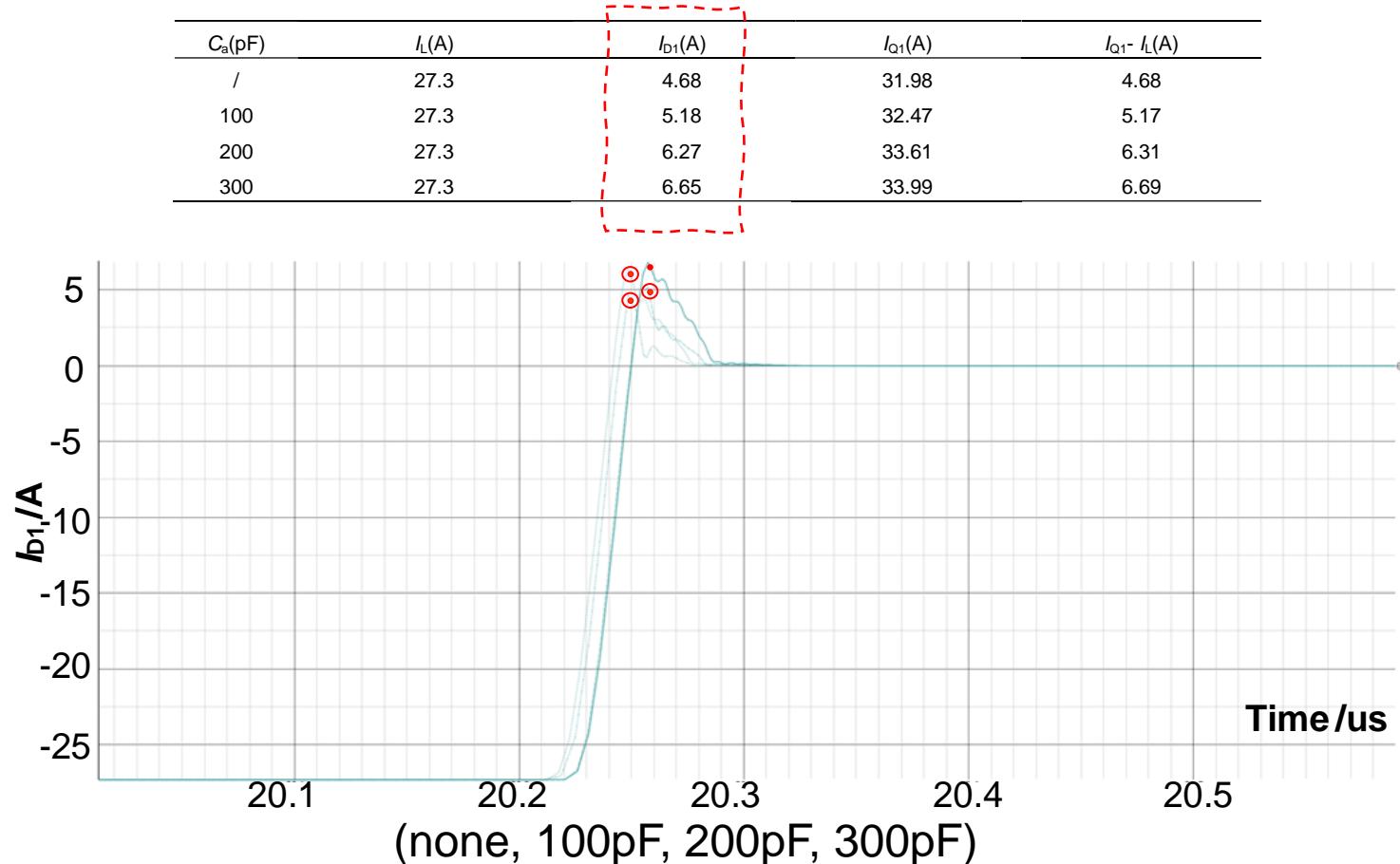- Effect of parasitic capacitance of the freewheeling diode
- Overall, as the diode parallel capacitance increases, the equivalent ‘reverse recovery current’ increases



SPICE model-based simulation of SIC-MOS turn-on

- Effect of parasitic capacitance of the switching arm
- the switching current I_{Q1} also tends to increase with the increase of C_b , which is mainly due to the parasitic capacitance of the MOS discharging to the channel at the on-time instant

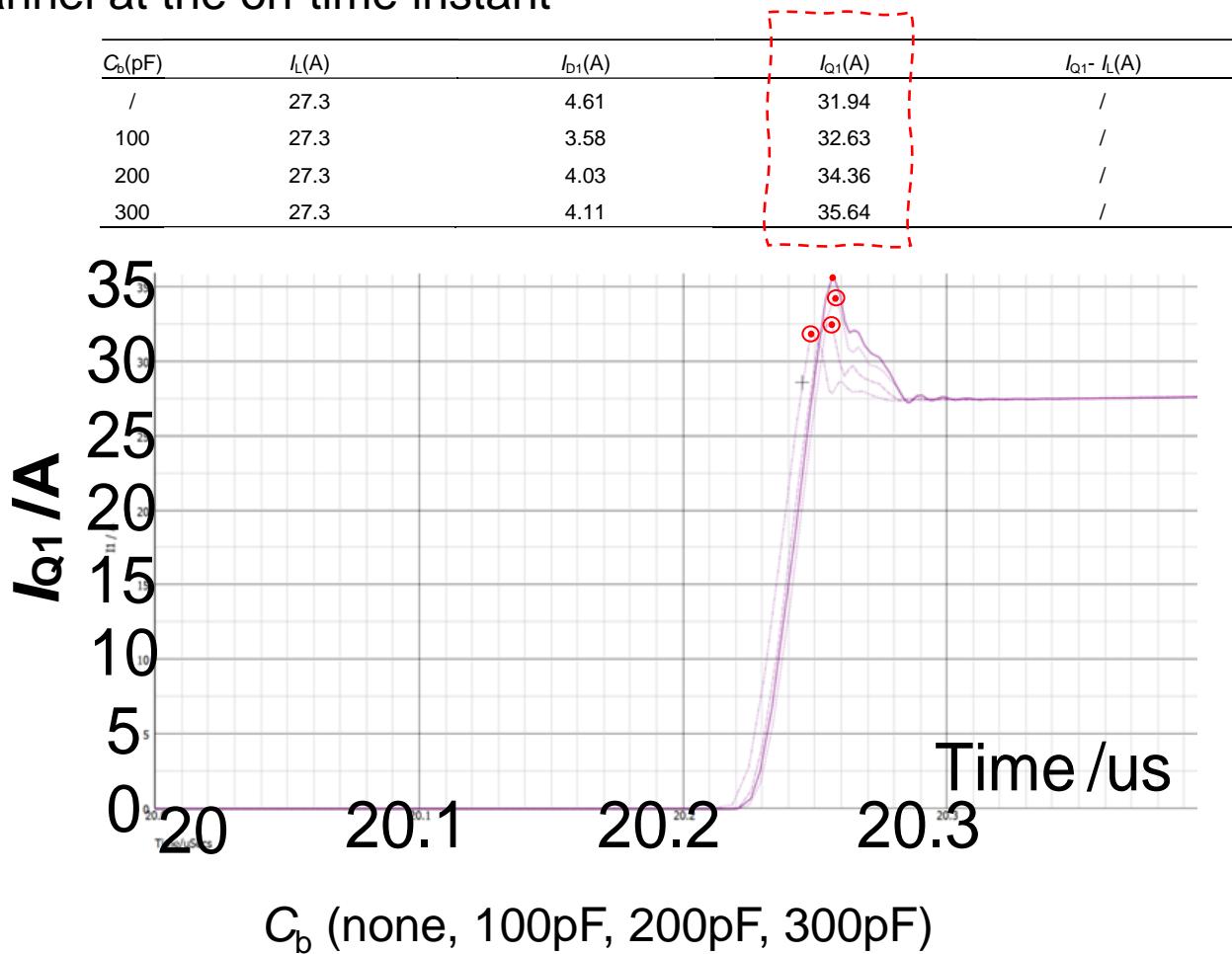
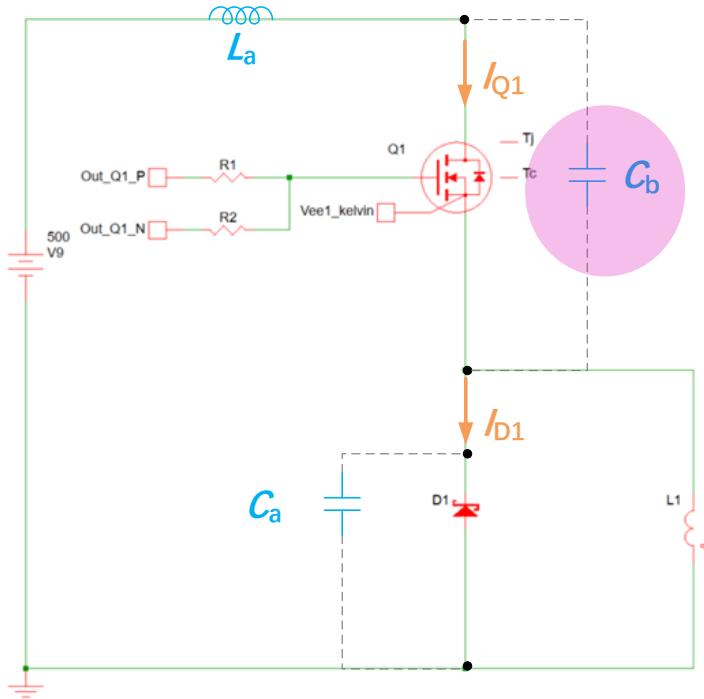


Table of contents

1

Switch on current overshoot

2

Switching current oscillation

3

Effect of parasitic capacitance

4


Effect of parasitic inductance

5

Summary



Switching current oscillation

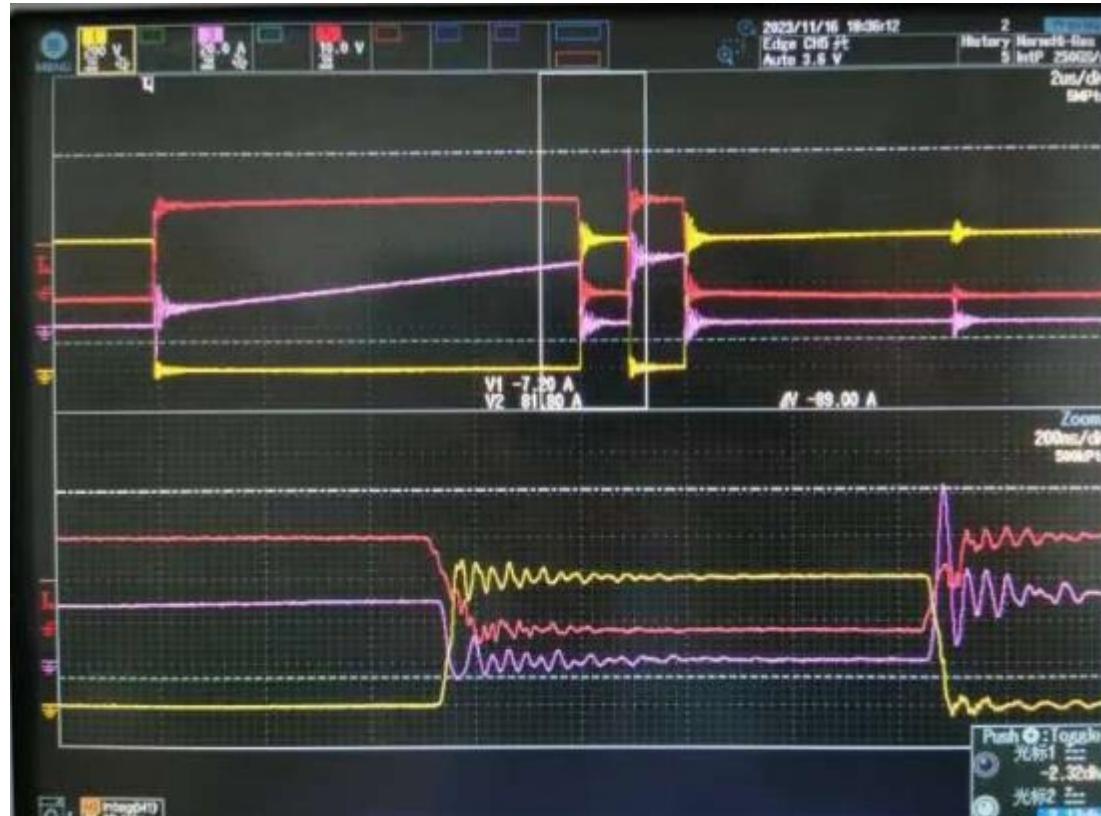- SiC current oscillations are often encountered when using SiC devices





Switching current oscillation

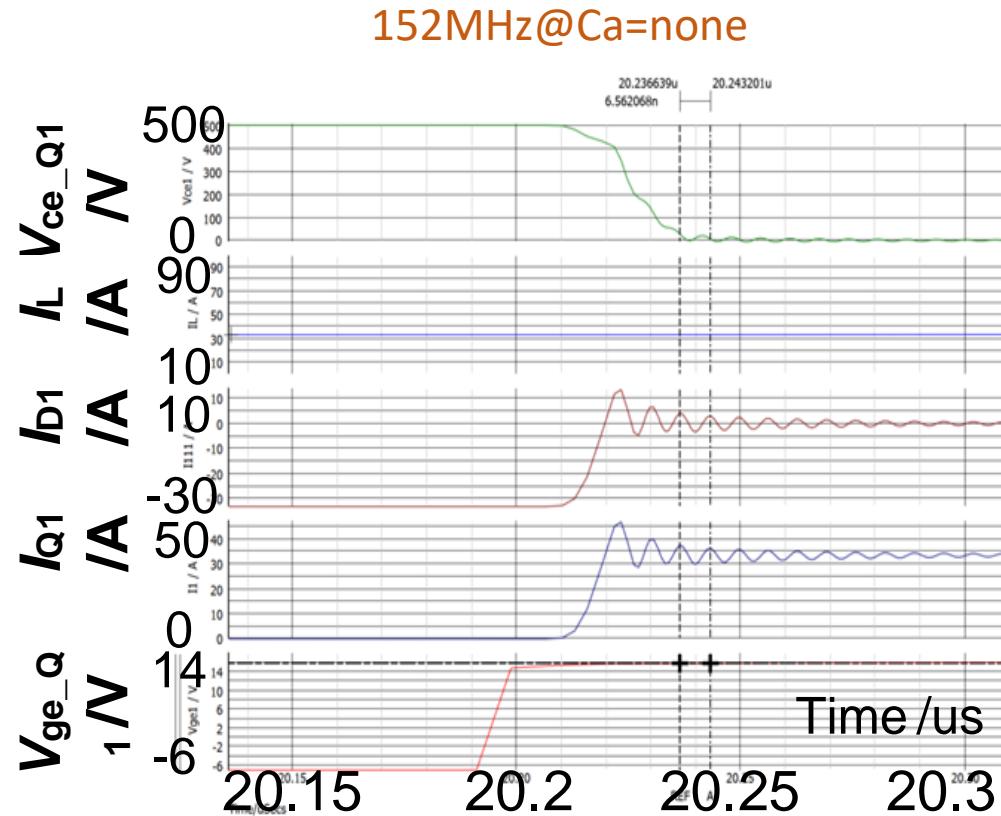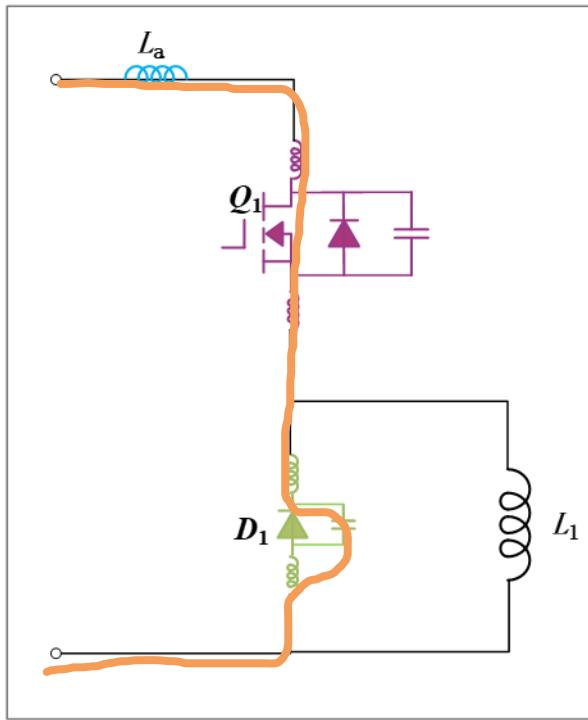- Impact of freewheeling switch (or AC/bus-) Parasitic Capacitance on Oscillation



Switching current oscillation

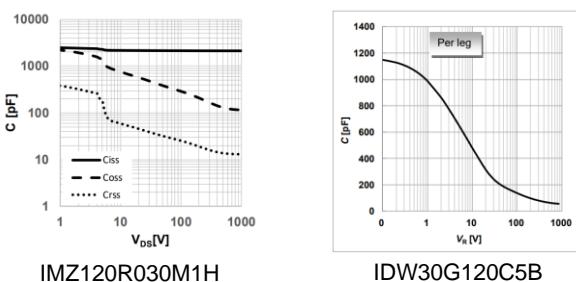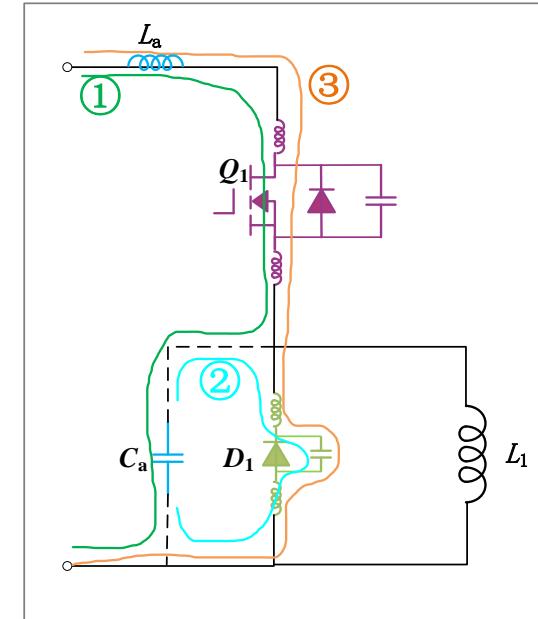- Impact of freewheeling switch (or AC/bus-) Parasitic Capacitance on Oscillation




$$f = \frac{1}{2\pi\sqrt{LC}}$$

C_a (pF)	L_a (nH)	C_{equ} (pF)	L_{equ} (nH)	f_{sim} (kHz)	$f_{cal-loop1}$ (kHz)	$f_{cal-loop2}$ (kHz)	$f_{cal-loop3}$ (kHz)
/	/	60	13 6.5	151	/	/	147
100	/	60	13 6.5	139	140	322	147
200	/	60	13 6.5	99	99	291	147
300	/	60	13 6.5	81	81	279	147
/	15	60	15 13 6.5	107	/	/	111
100	15	60	15 13 6.5	82	95	322	111
200	15	60	15 13 6.5	66	67	291	111
300	15	60	15 13 6.5	58	54	279	111
/	30	60	30 13 6.5	87	/	/	92
100	30	60	30 13 6.5	64	76	322	92
200	30	60	30 13 6.5	52	54	291	92
300	30	60	30 13 6.5	47	44	279	92

Fig. 9 Parasitic capacitance versus voltage curve

Switching current oscillation

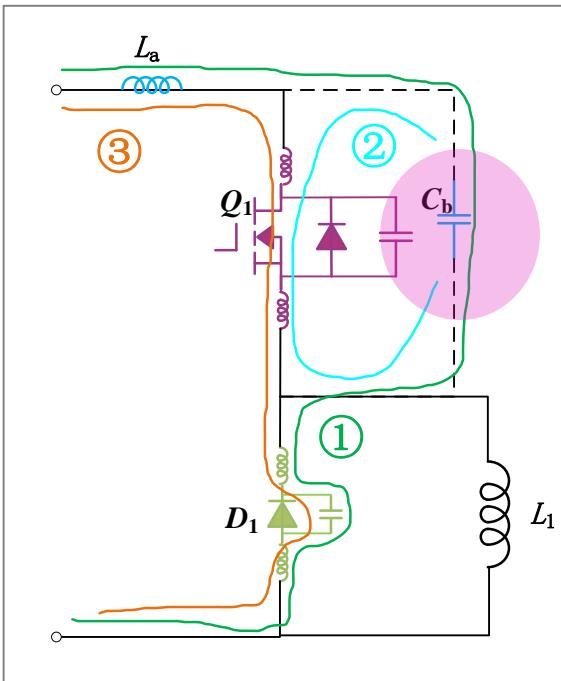- Impact of switch (or AC/bus +) parasitic capacitance on oscillation



C_b (pF)	L_a (nH)	C_{equ} (pF)	L_{equ} (nH)	f_{sim} (kHz)	$f_{cal-loop1}$ (kHz)	$f_{cal-loop2}$ (kHz)	$f_{cal-loop3}$ (kHz)
/	/	60	13 6.5	152	/	/	147
100	/	60	13 6.5	144	322	140	147
200	/	60	13 6.5	134	291	99	147
300	/	60	13 6.5	129	279	81	147
/	15	60	15 13 6.5	108	/	/	111
100	15	60	15 13 6.5	112	177	140	111
200	15	60	15 13 6.5	116	160	99	111
300	15	60	15 13 6.5	125	153	81	111
/	30	60	30 13 6.5	87	/	/	92
100	30	60	30 13 6.5	91	136	140	92
200	30	60	30 13 6.5	91	123	99	92
300	30	60	30 13 6.5	81	118	81	92

Table of contents

1

Switch on current overshoot

2

Switching current oscillation

3

Effect of parasitic capacitance

4


Effect of parasitic inductance

5

Summary


Effect of parasitic capacitance on SiC MOS switch performance

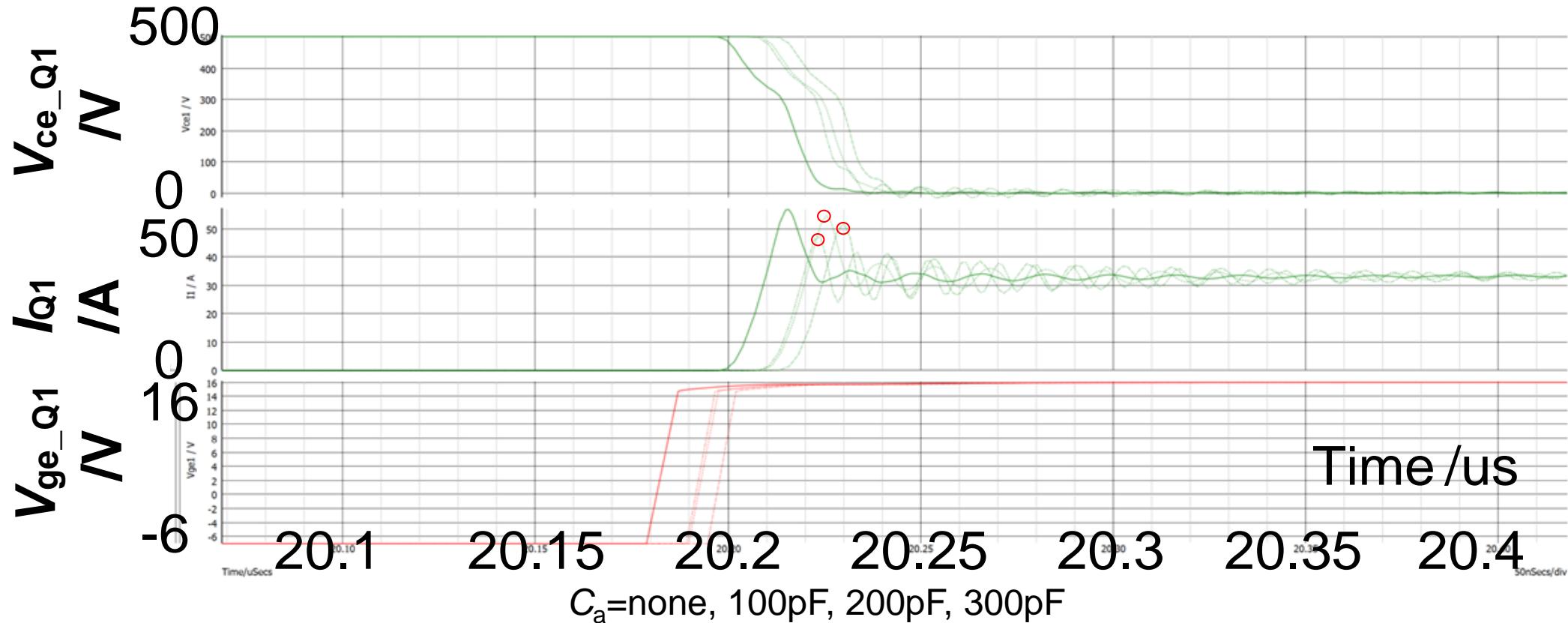- As the capacitance C_a increases, the frequency of oscillations decreases, and the peak value of the overcharge current increases.




Effect of parasitic capacitance on switching losses

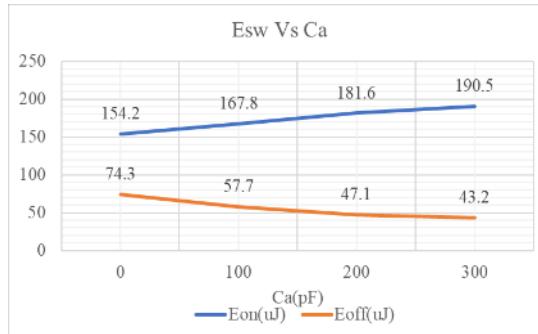- As the capacitance C_a/C_b increases, the turn-on loss becomes larger, and the turn-off loss decreases



C_a (pF)	I_L (A)	L_a (nH)	f_{sim} (kHz)	I_{on_peak} (A)	E_{on} (uJ)	E_{off} (uJ)
/	33A	15	107	47.9A	154.2	74.3
100	33A	15	82	52.4A	167.8	57.7
200	33A	15	66	55.1A	181.6	47.1
300	33A	15	58	56.9A	190.7	43

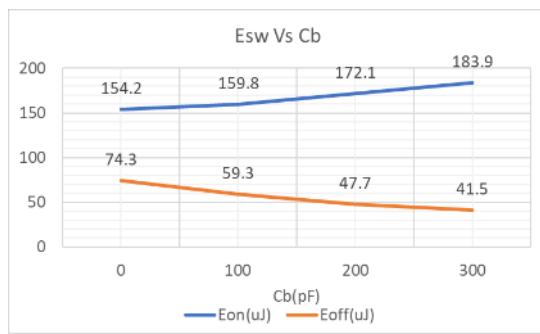

C_b (pF)	I_L (A)	L_a (nH)	f_{sim} (kHz)	I_{on_peak} (A)	E_{on} (uJ)	E_{off} (uJ)
/	33A	15nH	108	47.9	154.2	74.3
100pF	33A	15nH	112	50.9	159.8	59.3
200pF	33A	15nH	116	53.3	172.1	47.7
300pF	33A	15nH	125	55.9	183.9	41.5

Table of contents

1

Switch on current overshoot

2

Switching current oscillation

3

Effect of parasitic capacitance

4


Effect of parasitic inductance

5

Summary

Effect of parasitic inductance on SiC MOS switch performance

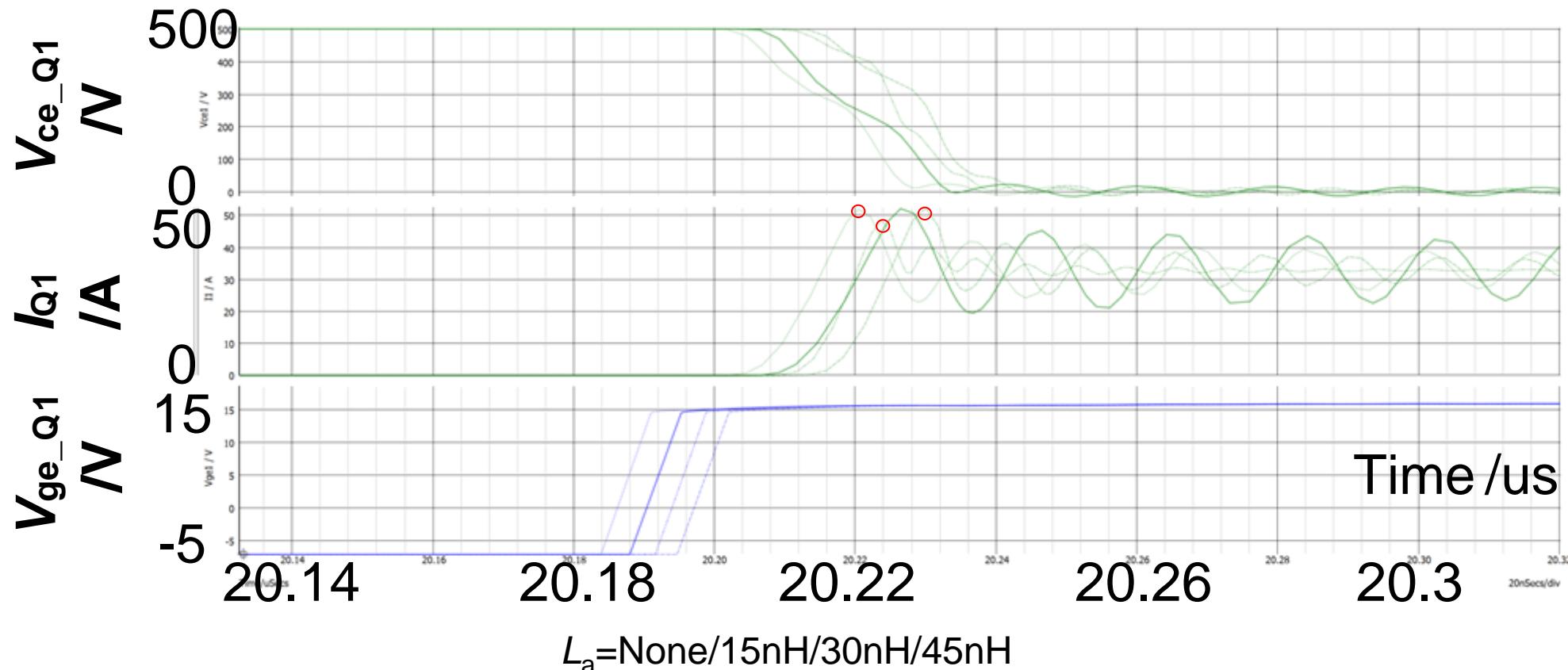- With the increase of inductance L_a , the frequency of the oscillations decreases, the amplitude of oscillations is larger, and the speed of oscillations' attenuation



Effect of parasitic inductance on switching losses

- Turn-on loss decreases and the turn-off loss increases as L_a increases

C_b (pF)	I_L (A)	L_a (nH)	f_{sim} (kHz)	I_{on_peak} (A)	E_{on} (uJ)	E_{off} (uJ)
100pF	33A	/	139	49.8	193.7	50.7
100pF	33A	15nH	83	51.9	166.9	57.4
100pF	33A	30nH	64	53.5	145.3	63.3
100pF	33A	45nH	53	53.2	129.7	68.4

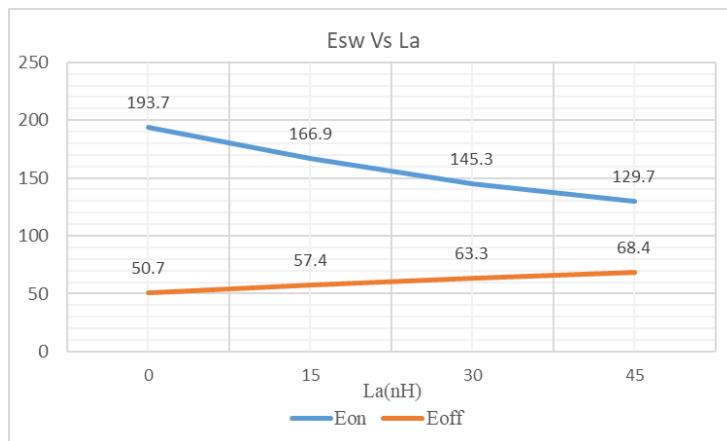


Table of contents

1

Switch on current overshoot

2

Switching current oscillation

3

Effect of parasitic capacitance

4

Effect of parasitic inductance

5

Summary

Effect of parasitic inductance on switching losses

- **Over-current** during switch turn-on in SiC-MOS devices is **caused by the discharge** of switch bridge arm parasitic capacitance **and charging** of freewheeling diode bridge arm parasitic capacitance
- High-speed switching causes turn-on **current oscillation** due to the **resonance of parasitic inductance and capacitance** in the system circuit.
- System parasitic **inductance decreases** turn-on losses but **increases** turn-off losses, while system parasitic **capacitance has the opposite effect**.
- To optimize efficiency, designers need to pay attention to the negative impact of parasitic capacitance on turn-on losses in SiC devices during the design phase.

Thank you for your attention and time.